




Optimal circuits for Streamed Linear Permutations Using RAM

François Serre, Thomas Holenstein, and Markus Püschel

Motivation: Folding FFTs


Pease FFT on n elements

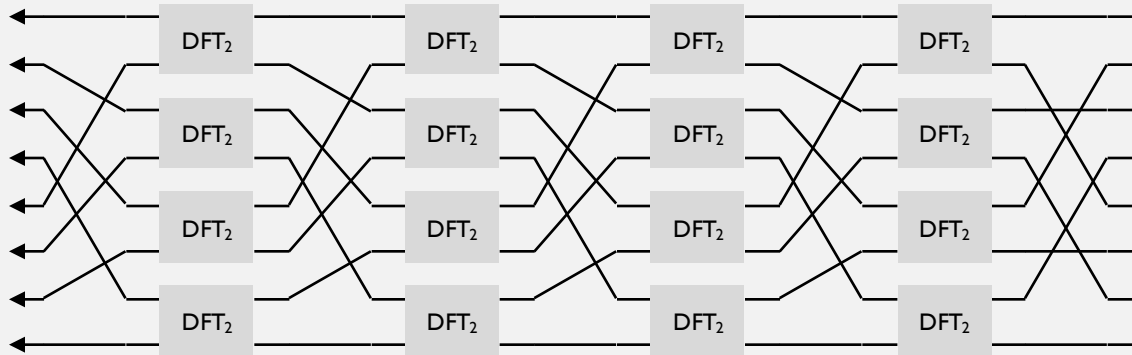

Area: $O(n \log n)$

Throughput: $n \frac{\text{samples}}{\text{cycle}}$

 Pease FFT on n elements, folded with w ports




Area: $O(w \log n)$

Throughput: $w \frac{\text{samples}}{\text{cycle}}$

We generate switching-optimal Verilog designs for these permutations


Overview of our method

 

Problem is phrased as a matrix factorization

Bit reversal is a “linear” permutation

Bit reversal on 8 elements

 


$$\begin{array}{ccc}
 \begin{pmatrix} 1 \\ 0 \\ 0 \end{pmatrix} & \mapsto & \begin{pmatrix} 0 \\ 0 \\ 1 \end{pmatrix} \\
 \begin{pmatrix} 1 \\ 1 \\ 1 \end{pmatrix} & \mapsto & \begin{pmatrix} 1 \\ 1 \\ 1 \end{pmatrix} \\
 \begin{pmatrix} 0 \\ 1 \\ 1 \end{pmatrix} & \mapsto & \begin{pmatrix} 1 \\ 1 \\ 0 \end{pmatrix} \\
 \uparrow & & \uparrow \\
 x & & P \cdot x
 \end{array}$$

$$P = \begin{pmatrix} & & 1 \\ & 1 & \\ 1 & & \end{pmatrix}$$

A permutation is linear if it maps linearly the bits of its addresses

Other linear permutations

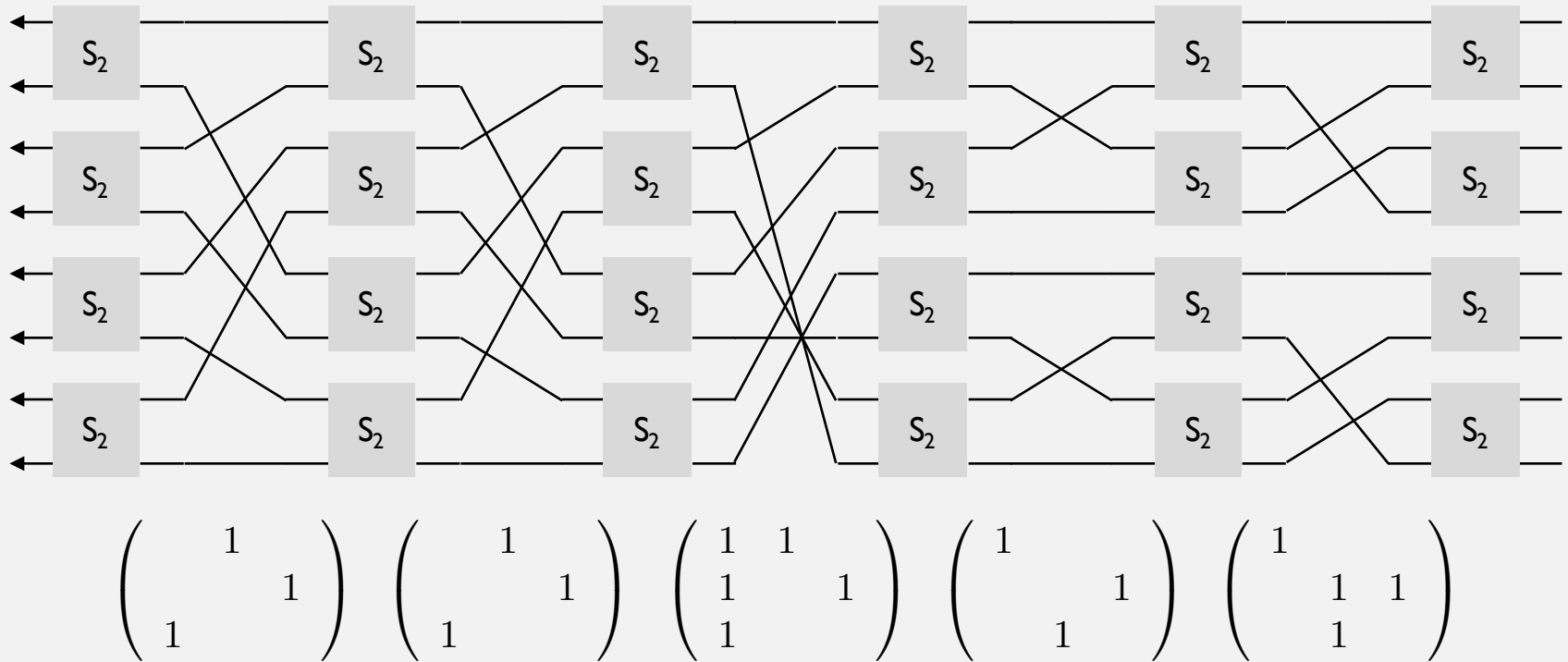A streaming sorting network (M. Zuluaga et al.)




Other linear permutations

- ✓ Identity
- ✓ Bit reversal
- ✓ Stride permutations (perfect shuffle, matrix transpositions)
- ✓ Hadamard reordering
- ✓ Gray code reordering

Most permutations used in signal processing algorithms are linear


Blocking the matrix

 Bit-reversal on $2^n = 8$ elements, $2^t = 4$ cycles, $2^k = 2$ ports



$$P = \left(\begin{array}{c|c} & 1 \\ \hline 1 & \end{array} \right)$$

 Bit-reversal on $2^n = 8$ elements, $2^t = 2$ cycles, $2^k = 4$ ports



$$P = \left(\begin{array}{c|c} & 1 \\ \hline 1 & \end{array} \right)$$

Why?

A lower bound on the number of switches

Theorem

Considering $P = \begin{pmatrix} P_4 & P_3 \\ P_2 & P_1 \end{pmatrix}$ such that P_1 is $k \times k$,


Implementing P with 2^k ports requires at least $2^{k-1} \text{rk } P_2$ switches.

Proof: see paper



Blocking the matrix

 
Bit-reversal on $2^n = 8$ elements, $2^t = 4$ cycles, $2^k = 2$ ports



$$P = \left(\begin{array}{c|c} & 1 \\ \hline & 1 \\ \hline 1 & \end{array} \right)$$

Requires 1 switch

 Bit-reversal on $2^n = 8$ elements, $2^t = 2$ cycles, $2^k = 4$ ports




$$P = \left(\begin{array}{c|c} & 1 \\ \hline & 1 \\ \hline 1 & \end{array} \right)$$

Requires 2 switches

This bound is sharp!


Related Work

RAM/SNW/RAM

 

- Milder et al., *Automatic generation of streaming datapaths for arbitrary fixed permutations*, DATE'09
- Chen et al., *Automatic generation of high throughput energy efficient streaming architectures for arbitrary fixed permutations*, FPL'15

SNW/RAM/SNW

 


- Püschel et al., *Permuting streaming data using RAMs*, JACM'09
- Chen et al., *Energy and memory efficient mapping of bitonic sorting on FPGA*, FPGA'15

We use the same blocks


Building blocks

Spatial permutations – Switching network

 

Implementation uses 2^{k-1} $k \times k$ switches

Temporal permutations – Memory banks

 


Total memory capacity: the dataset size

We need to decompose a general matrix into these.

General linear permutation

RAM/SNW/RAM

 


$$\begin{pmatrix} P_4 & P_3 \\ P_2 & P_1 \end{pmatrix} = \begin{pmatrix} L_4 & L_3 \\ & I_k \end{pmatrix} \cdot \begin{pmatrix} I_t & \\ C_2 & C_1 \end{pmatrix} \cdot \begin{pmatrix} R_4 & R_3 \\ & I_k \end{pmatrix}$$

$2^{k-1} \text{ rk } P_2$ switches

Example: bit reversal: 1 switch

$$\left(\begin{array}{c|c} & 1 \\ \hline 1 & \\ \hline 1 & \end{array} \right) = \left(\begin{array}{c|c} 1 & 1 \\ \hline & 1 \\ \hline & \end{array} \right) \left(\begin{array}{c|c} 1 & \\ \hline 1 & 1 \\ \hline \end{array} \right) \left(\begin{array}{c|c} 1 & 1 \\ \hline & 1 \\ \hline \end{array} \right)$$

SNW/RAM/SNW

 

$$\begin{pmatrix} P_4 & P_3 \\ P_2 & P_1 \end{pmatrix} = \begin{pmatrix} I_t & \\ L_2 & L_1 \end{pmatrix} \cdot \begin{pmatrix} C_4 & C_3 \\ & I_k \end{pmatrix} \cdot \begin{pmatrix} I_t & \\ R_2 & R_1 \end{pmatrix}$$

$2^{k-1} \max(\text{rk } P_2, n - \text{rk } P_4 - \text{rk } P_1)$ switches

Example: bit reversal: 2 switches


$$\left(\begin{array}{c|c} & 1 \\ \hline 1 & \\ \hline 1 & \end{array} \right) = \left(\begin{array}{c|c} 1 & 1 \\ \hline & 1 \\ \hline \end{array} \right) \left(\begin{array}{c|c} 1 & 1 \\ \hline & 1 \\ \hline \end{array} \right) \left(\begin{array}{c|c} 1 & 1 \\ \hline 1 & 1 \\ \hline \end{array} \right)$$

In both cases, an optimal decomposition can be computed in $O(n^3)$

Results

Bit-reversal, $2^n = 2048$ on Xilinx Virtex-7 FPGA


Throughput [Gbits/s]

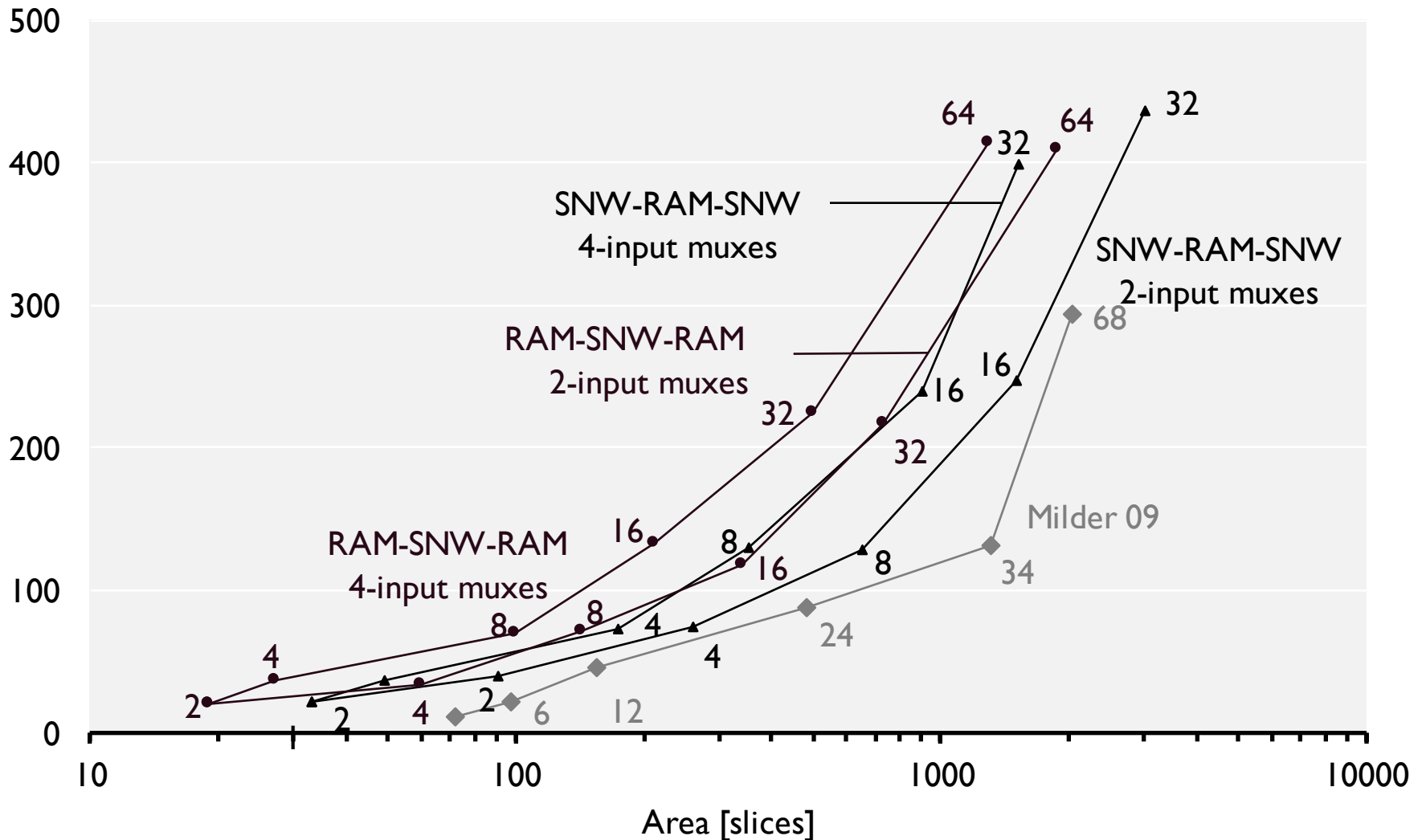

Conclusion


- Exact routing complexity of streaming linear permutations
- Two architectures:

RAM/SNW/RAM

 

- Always switching optimal
- Uses a memory capacity of twice the dataset

RAM/SNW/RAM

 

- Almost always switching optimal
- Uses a memory capacity equal to the dataset